
Contents

Preface	xi
Chapter 1. Nonlinear Two-terminal Devices	1
1.1. Introduction	1
1.2. Example of a nonlinear two-terminal device – the diode.	2
1.3. Characteristic of a diode	3
1.3.1. Real diode	3
1.3.2. Diode in first approximation	4
1.3.3. Ideal diode – second approximation.	5
1.4. Design of a thresholdless diode.	6
1.4.1. Positive input voltage	7
1.4.2. Negative input voltage	7
1.5. Load line and operating point.	8
1.6. Other nonlinear components	10
1.6.1. Thermistors or NTC (Negative Temperature Coefficient)	10
1.6.2. Photoresistors	11
1.6.3. Varicap diodes or variable capacitance diodes	12
1.7. Nonlinear applications of the diode	13
1.7.1. Half-wave rectification	13
1.7.2. Full-wave rectification with diode bridge.	16
1.7.3. Peak clipping	23
1.7.4. Peak detector	24
1.7.5. Recovery circuits	25
1.7.6. Influence of dynamic and reverse resistances on the recovery of the continuous component of a signal	28

1.7.7. Logarithmic amplifier	36
1.7.8. Anti-logarithmic amplifier	37
1.7.9. Logic functions with diodes	39
1.8. Exercises	42
1.9. Solutions to exercises	54
Chapter 2. Low-frequency Oscillators	83
2.1. Feedback study	83
2.1.1. Negative feedback	84
2.1.2. Positive feedback	85
2.1.3. Oscillators and positive feedback	85
2.2. Principle of sinusoidal feedback oscillator	87
2.3. Oscillator parameters	87
2.4. Linear mode oscillator operation	88
2.4.1. Introduction	88
2.4.2. Feedback oscillator	88
2.5. Phase-shift oscillators	91
2.5.1. Schematic diagram and equation	91
2.5.2. Low-pass cells	94
2.5.3. High-pass cells	96
2.5.4. Phase-shift oscillator with operational amplifier	97
2.5.5. RC oscillators with transistors	98
2.6. Bridge oscillator	105
2.6.1. Principle	105
2.6.2. Principle of the bridge oscillator with operational amplifier	106
2.6.3. Study of the bridge oscillator in the general case	107
2.6.4. Study of Wien bridge oscillator	108
2.6.5. Study of the Wien bridge oscillator as one feedback branch oscillator	111
2.7. Band-pass filter oscillator	113
2.7.1. Feedback circuit	113
2.7.2. Oscillator circuit	114
2.7.3. Oscillation frequency	115
2.7.4. Condition for sustained oscillation	116
2.8. Generator of sinusoidal waves with shaper	116
2.8.1. Principle	116
2.8.2. Generation of the triangle wave	117
2.8.3. Shaper circuit	120
2.8.4. Shaper operation	120
2.8.5. Frequency of the output signal	121

Chapter 3. High-frequency Oscillators	125
3.1. Elementary high-frequency oscillator	125
3.1.1. Equation	125
3.1.2. Study of the evolution of output voltage: sinusoidal condition	129
3.2. High-frequency oscillators with discrete components	133
3.2.1. Introduction	133
3.2.2. Equivalent diagram of the bipolar transistor	133
3.3. Study of oscillators with bipolar transistors	134
3.3.1. Operating equation	134
3.3.2. Example of passive linear quadripole	138
3.4. Oscillator case study: Colpitts oscillator.	139
3.4.1. Presentation	139
3.4.2. Operating equation of Colpitts oscillator	140
3.4.3. Parameters of feedback quadripole	143
3.4.4. Oscillation frequency and condition for sustained oscillation	144
3.5. Hartley oscillator.	146
3.5.1. Schematic diagram	146
3.5.2. Parameters of the feedback circuit.	147
3.5.3. Operating equation	148
3.5.4. Oscillation frequency	148
3.5.5. Condition for sustained oscillation	149
3.6. Clapp oscillator	150
3.6.1. Schematic diagram	150
3.6.2. Operating equation	150
3.6.3. Characteristic parameters of the oscillator	152
3.7. Quartz crystal oscillator	153
3.7.1. Frequency stability of an oscillator	153
3.7.2. Quartz crystal operation	156
3.7.3. Equivalent impedance of quartz crystal	157
3.7.4. Frequency behavior of a quartz crystal	159
3.7.5. Example of quartz crystal oscillator.	163
Chapter 4. Oscillator as a Nonlinear Device	171
4.1. Introduction	171
4.2. Stability of an oscillator	174
4.2.1. Static stability	174
4.2.2. Dynamic stability	175
4.3. Nonlinear phenomena in oscillators	176

4.4. Stabilization of the amplitude of output voltage	181
4.5. Amplitude of the output signal: first harmonic method.	183
4.5.1. Principle of the first harmonic method	183
4.5.2. Study of amplitude stabilization	184
4.6. Exercises	187
4.7. Solutions to exercises	204
Chapter 5. Circuits in Switching Mode	235
5.1. Basic elements	235
5.2. Behavior of a capacitor in a circuit.	236
5.3. RC circuits in switching mode	239
5.3.1. Case of a low-pass cell – integrating circuit	239
5.3.2. Case of a high-pass cell – differentiating circuit	245
5.4. Bipolar transistor in switching mode.	250
5.4.1. Bipolar transistor characteristics.	250
5.4.2. Operation in switching mode	252
5.4.3. Logical functions with a switching transistor	253
Chapter 6. Astable Multivibrators	255
6.1. Introduction	255
6.2. Astable multivibrator with transistors	255
6.2.1. Introduction	255
6.2.2. Principle	256
6.2.3. Operating condition.	257
6.2.4. Operation	258
6.2.5. Period of the output signal	261
6.3. Astable device with operational amplifier.	262
6.3.1. Operating principle	263
6.3.2. Period of the output signal	265
6.4. Astable circuit with voltage-controlled frequency	266
6.4.1. Principle and operation	266
6.4.2. Period of the output signal	268
6.5. Timer-based astable circuit (555 integrated circuit)	271
6.5.1. Presentation of 555 timer.	271
6.5.2. Operating principle of the 555-based astable circuit.	273
6.5.3. Period of the output signal	275
6.5.4. Another possible implementation	277
6.6. Astable multivibrators with logic gates	278
6.6.1. Principle and operation	278
6.6.2. Period of the output signal	281

6.7. Astable multivibrators with specialized integrated circuits	283
6.7.1. Introduction	283
6.7.2. Specification of the 74123 integrated circuit	283
6.7.3. Astable circuit based on a 74123 integrated circuit	285
6.7.4. Other specialized circuits.	287
6.8. Exercises	289
6.9. Solutions to exercises	301
References	345
Index	347