
Contents

Preface	ix
Chapter 1. Flip-flops	1
1.1. Overview of the different types of flip-flops	1
1.2. Monostable flip-flops	3
1.2.1. Monostable transistor flip-flop	3
1.2.2. Operational amplifier monostable flip-flop	6
1.2.3. Logic gate monostable flip-flop	11
1.2.4. Timer monostable flip-flop: 555 integrated circuit	15
1.3. Bistable circuits	17
1.3.1. Transistor bistable	17
1.3.2. Improved bipolar transistor bistable	20
1.3.3. Practical example of transistor bistable: the “SR” flip-flop	21
1.3.4. “SR” flip-flop and logic gate derivatives	22
1.3.5. Integrated circuit “JK” bistable flip-flop	23
1.4. The Schmitt flip-flop	25
1.4.1. Principle of the Schmitt flip-flop	25
1.4.2. Operation of a Schmitt trigger	26
1.4.3. Transistor Schmitt trigger	27
1.4.4. Operational amplifier Schmitt trigger	32
1.4.5. The 555 Schmitt trigger	43
1.4.6. Schmitt trigger based on logic integrated circuits	45
1.5. Exercises on flip-flops	49

Chapter 2. Analog-to-Digital and Digital-to-Analog Converters	99
2.1. General information	99
2.1.1. Analog-to-digital converters	99
2.1.2. Digital-to-analog conversion	100
2.1.3. The different elements involved in the conversion	101
2.2. Analog/digital and digital/analog conversion	106
2.2.1. Introduction	106
2.2.2. Sample–hold	107
2.2.3. Influence of the sample-and-hold circuit on the signal spectrum	113
2.2.4. Quantification	116
2.3. Analog-to-digital converters	118
2.3.1. Introduction	118
2.3.2. Parallel analog-to-digital or flash converters	120
2.3.3. Successive approximations or weighing-based ADC	123
2.3.4. Pulse counting ADC	129
2.3.5. Voltage–frequency ADC	146
2.4. Digital-to-analog converters	149
2.4.1. Introduction	149
2.4.2. Weighted-resistor digital-to-analog converters	150
2.4.3. R-2R ladder network digital-to-analog converters	152
2.5. Exercises on DACs and ADCs	158
Chapter 3. The Phase-locked Loop (PLL)	191
3.1. Introduction	191
3.2. Relationship between frequency and instantaneous phase	192
3.3. Origin of the phase-locked loop	194
3.3.1. Amplitude modulation principle	195
3.3.2. Amplitude demodulation principle	196
3.3.3. Synchronous demodulation principle	198
3.4. Phase-locked loop (PLL)	199
3.4.1. Advantages of the phase-locked loop	199
3.4.2. PLL principle and operation	200
3.5. Study of the elements that constitute a PLL	207
3.5.1. The phase comparator	207
3.5.2. Low-pass filter	225
3.5.3. Voltage-controlled oscillator (VCO)	230
3.6. Examples of integrated PLL	240
3.6.1. 4046 IC-based PLL	240
3.6.2. The 565 and 567 IC-based PLL	245

3.7. PLL block diagram	248
3.8. Study of the behavior of a PLL	250
3.8.1. PLL transfer function	250
3.8.2. Behavior of the PLL according to filter type	252
3.9. Applications for PLLs	260
3.9.1. Frequency multiplication	261
3.9.2. Frequency synthesis	263
3.9.3. Frequency modulation and demodulation	264
3.9.4. Frequency hopping-based or FSK (frequency shift keying) demodulation	266
3.10. Exercises on PLLs	270
References	311
Index	313